

EE236: Experiment No.1

I-V characteristic of different diodes and finding the ideality factor

Narne Avinash Chowadry,200070047

August 12, 2022

1 Overview of the experiment

1.1 Aim of the experiment

To plot the IV characteristic of normal diode, Zener and colour led's and observe their patterns and obtain the ideality factor using the slope of the \ln curve.

1.2 Methods

Voltage across the diode is varied using a potentiometer, that voltage and current through the diode is measured for every interval of 0.1v or 0.2v, Then plot a graph for $\ln(i)$ vs V , slope can be obtained for the graph and using the formulae, we can obtain ideality factor.

$$\ln(I_D/I_0) + E_g/KT = qV_d/nKT$$


(1)

2 Design

1) A voltage of +5v is used connected to a 100ohm and 1Kohm in series.

2) Now our diode under observation and a 100ohm resistor in series connected across the potentiometer.

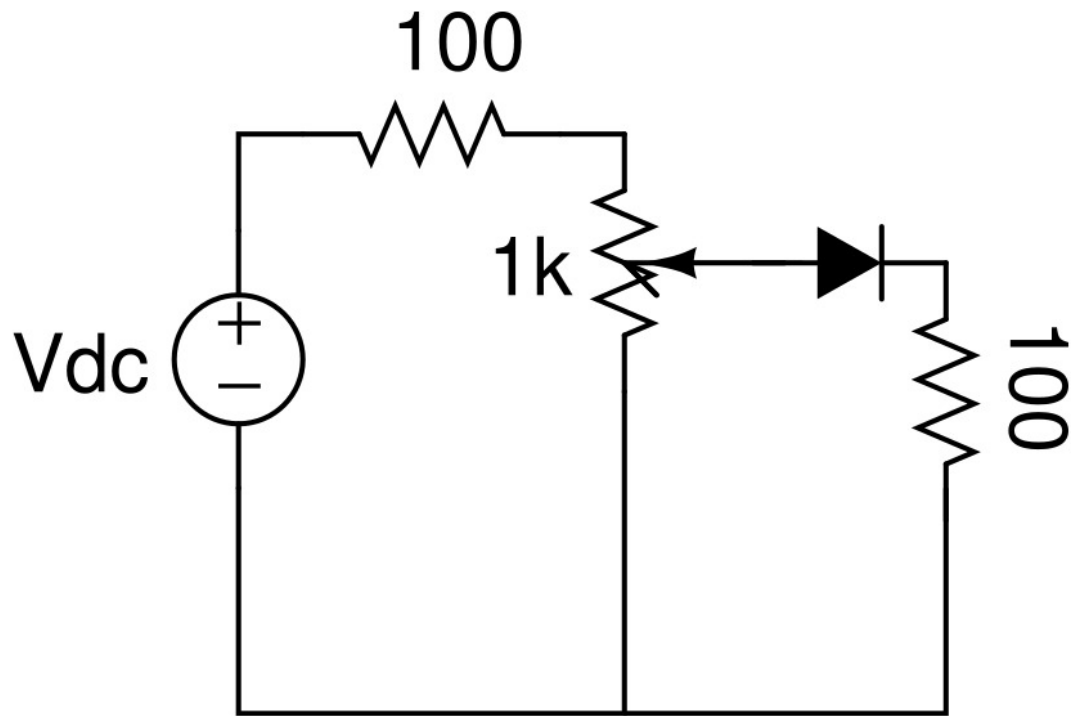3) Varying the potentiometer with small values voltage across the diode and current through the diode is measured and noted down



3 Simulation results

3.1 Code snippet

```
Diode Charecterstics
.include Diode1N914.txt
.include white_5mm.txt
.include yellow_5mm.txt
.include green_5mm.txt
.include red_5mm.txt
.include blue_5mm.txt
d1121n914
```

```

d213red
d314blue
d415green
d516yellow
d617white
v12120
v23130
v34140
v45150
v56160
v67170

```

```

r1 12 0 100
r2 13 0 100
r3 14 0 100
r4 15 0 100
r5 16 0 100
r6 17 0 100

```

```

v 1 0 dc 0


```


```

.dc v 0 5 0.001
.control
run
plot i(v1) vs v(1)-v(2) i(v2) vs v(1)-v(3) i(v3) vs v(1)-v(4) i(v4) vs v(1)-v(5)
i(v5) vs v(1)-v(6) i(v6) vs v(1)-v(7)
plot ln(abs(i(v1))) vs v(1)-v(2) ln(abs(i(v2))) vs v(1)-v(3) ln(abs(i(v3))) vs
v(1)-v(4) ln(abs(i(v4))) vs v(1)-v(5) ln(abs(i(v5))) vs v(1)-v(6) ln(abs(i(v6)))
vs v(1)-v(7)
.endc
.end


```


3.2 Simulation results

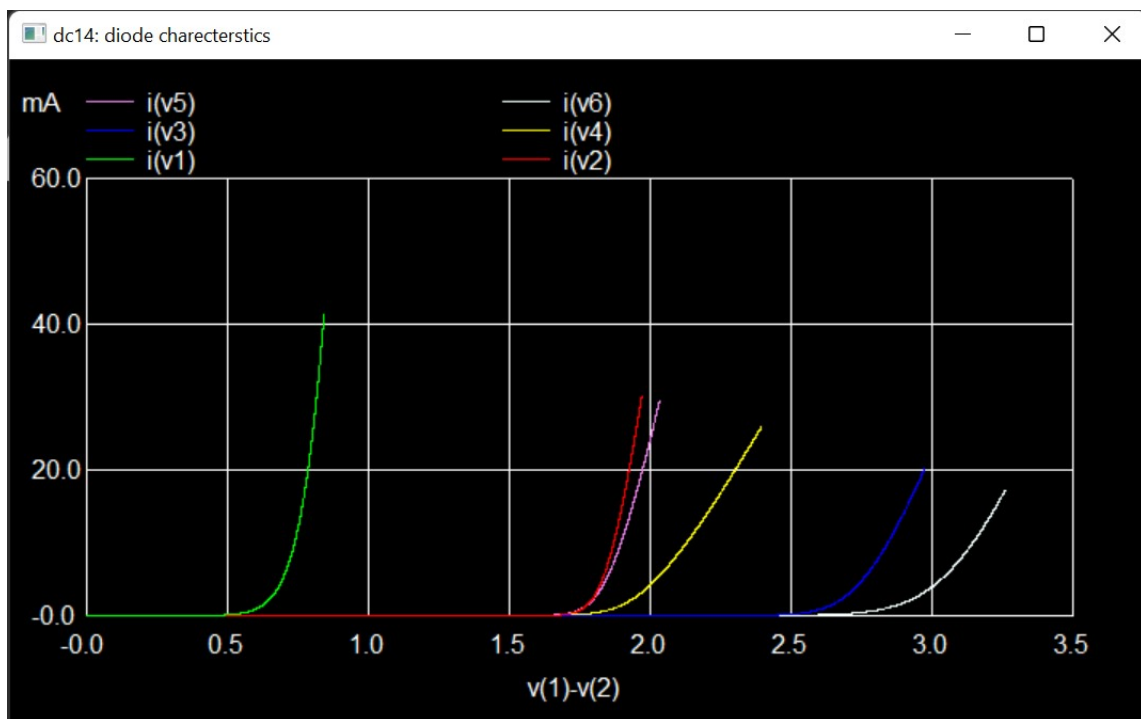

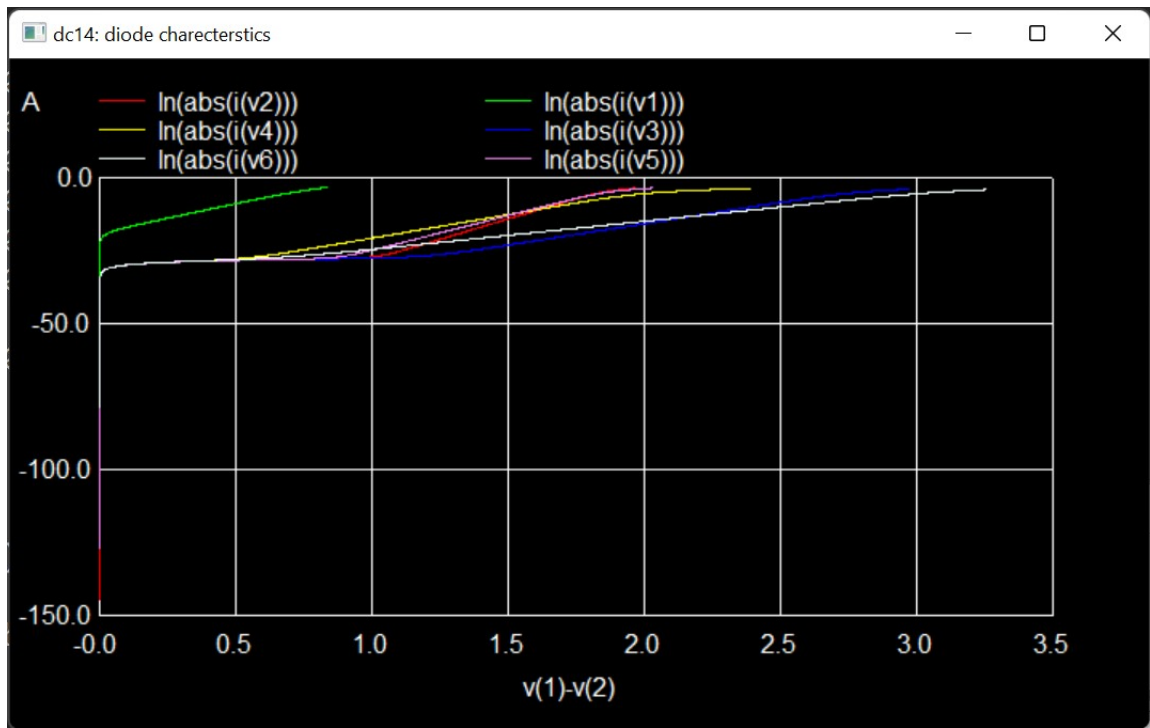

4 Experimental results

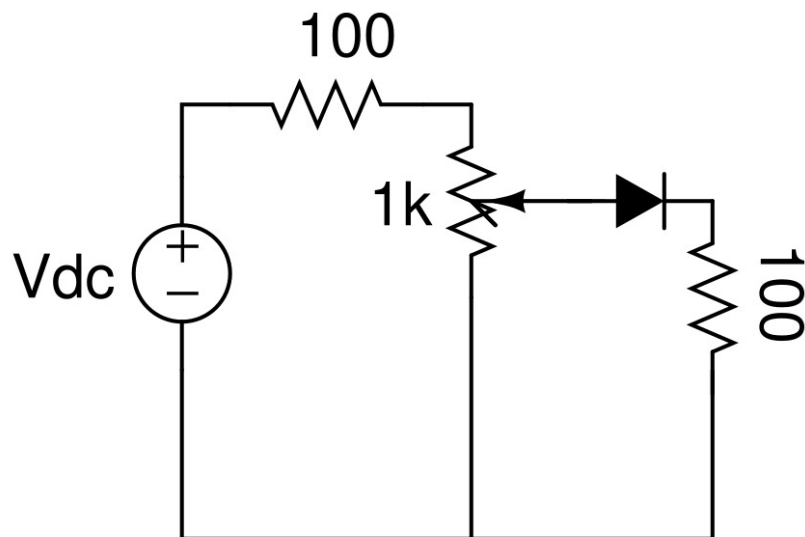

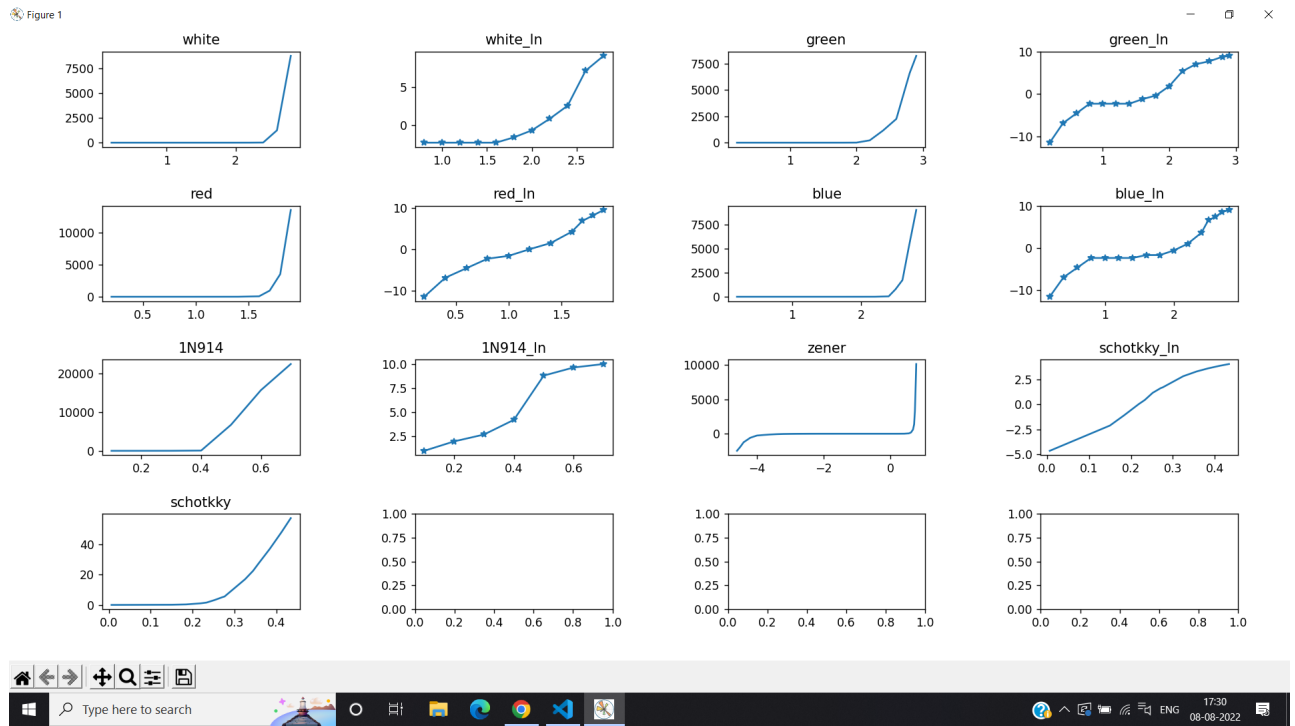

the values obtained are

```

4
5  x_w = [.2, .4, .6, .8, 1, 1.2, 1.4, 1.6, 1.8, 2.0, 2.2, 2.4, 2.6, 2.8]
6  y_w = [.00001, .001, .01, .1, .1, .1, .1, .1, .2, .5, 2.3, 12.8, 1245, 8760]
7  y_l_w = np.log([.1, .1, .1, .1, .1, .2, .5, 2.3, 12.8, 1245, 8760])
8
9
10 x_g = [.2, .4, .6, .8, 1, 1.2, 1.4, 1.6, 1.8, 2, 2.2, 2.4, 2.6, 2.8, 2.9]
11 y_g = [.00001, .001, .01, .1, .1, .1, .1, .3, .7, 6.4, 220, 1150, 2250, 6500]
12 y_l_g = np.log(y_g)
13
14
15 x_r = [.2, .4, .6, .8, 1, 1.2, 1.4, 1.6, 1.7, 1.8, 1.9]      #Voltage in V
16 y_r = [.00001, .001, .01, .1, .2, 1, 4.5, 70, 950, 3510, 13510]  # I in
17 y_l_r = np.log(y_r)
18
19
20 x_b = [.2, .4, .6, .8, 1, 1.2, 1.4, 1.6, 1.8, 2, 2.2, 2.4, 2.5, 2.6, 2.7,
21 y_b = [.00001, .001, .01, .1, .1, .1, .1, .2, .2, .6, 2.9, 40, 777, 1726,
22 y_l_b = np.log(y_b)
23
24 x_1N = [.1, .2, .3, .4, .5, .6, .7]      #Voltage in V
25 y_1N = [2.7, 7.2, 14.7, 67.7, 6750, 15720, 22500]  # I in microAmp
26 y_l_1N = np.log(y_1N)
27
28 x_z = [-4.6, -4.5, -4.4, -4.2, -4, -3.8, -3.6, -3.4, -3.2, -3, -2.8, -2.4,
29 y_z = [-2490, -1907, -1241, -586, -260, -180, -113, -64, -34.9, -22, -12.4
30
31 x_bat = [.0063, .150, .184, .219, .233, .252, .271, .276, .325, .344, .357
32 y_bat = [9.5, 120, 337, 1038, 1548, 3190, 5100, 5520, 16900, 22400, 27200,
33 y_bat = np.array(y_bat)/1000
34 v_l_hat = np.log(v_hat)

```

5 Experiment completion status

cutin voltages of simulation

d1 0.6v

red 1.2v

blue 2.5v

green 1.85v
yellow 1.75
white 2.9v

cutin voltages of experment

d1 0.5v
red 1.5v
blue 2.2v
green 1.3v
yellow 1.75
white 2.2v

Ideality factor:

White - 1.63
Green - 1.45
Blue - 1.49
Red - 1.47