

EE236: Experiment No. 6

Bipolar Junction Transistor

Narne Avinash , 200070047

October 8, 2022

1 Overview of the experiment

1.1 Aim of the experiment

- Measure the forward active and reverse active parameters in common base and common emitter configurations
- Plot the output DC characteristics in CE configuration.
- Plot combined I_C and I_B vs V_{BE} of a BJT on a semi-log scale (also called Gummel plot).
- Plot β_{DC} vs I_C characteristics for constant V_{BC} .
- Calculate r Pi model small signal parameters.

1.2 Methods

- We connected bjt with required common base,emmitter configurations accordingly and used 3 DMM's to measure required values
- Varied voltage and measured the required current and voltage parameters

2 Design

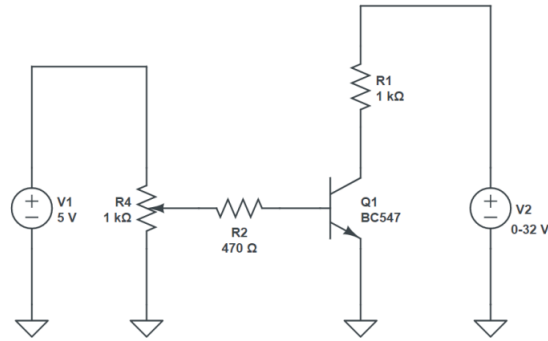


Figure 1: Circuit for measuring BJT Parameters in CE configuration

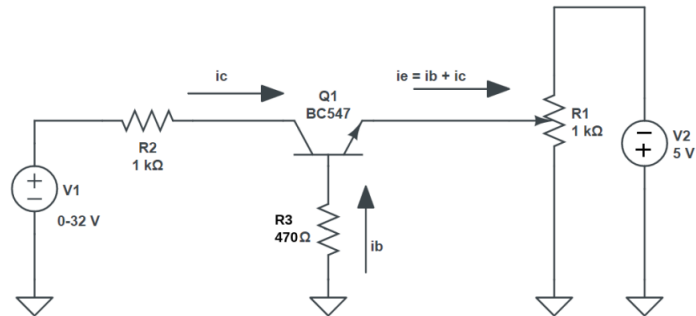


Figure 2: Circuit for measuring BJT Parameters in CB configuration

3 Simulations

3.1 Simulation results

BJT Parameters in CE configuration

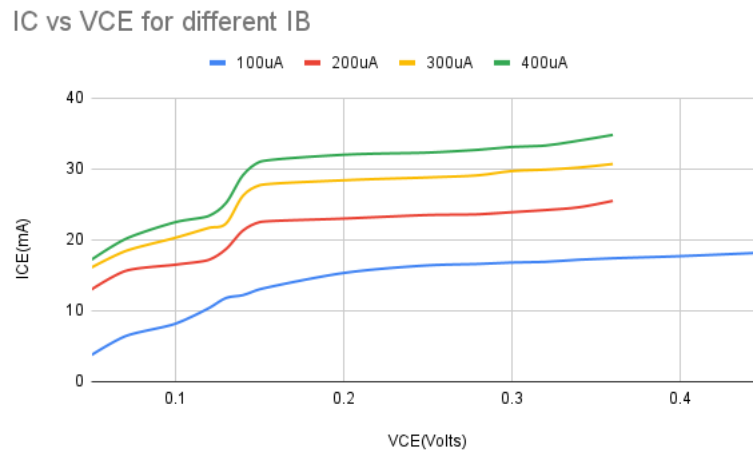


Figure 3: IC vs VCE for different IB

BJT Parameters in CB configuration

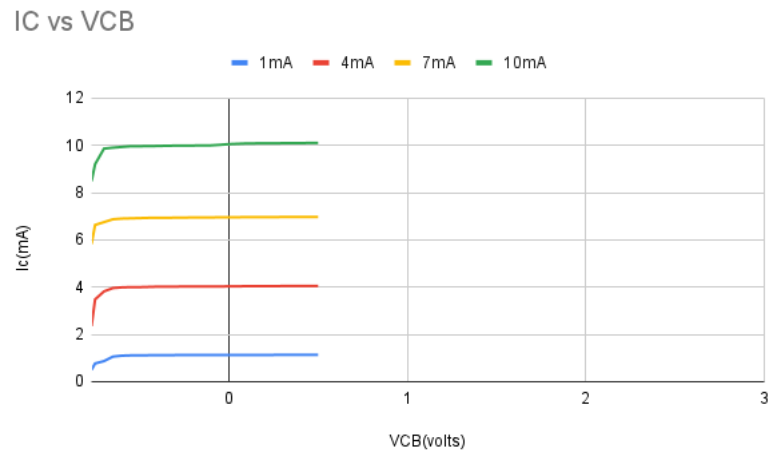


Figure 4: IC vs VCB for different IE

Gummel Plot

ic,ib vs Vbe

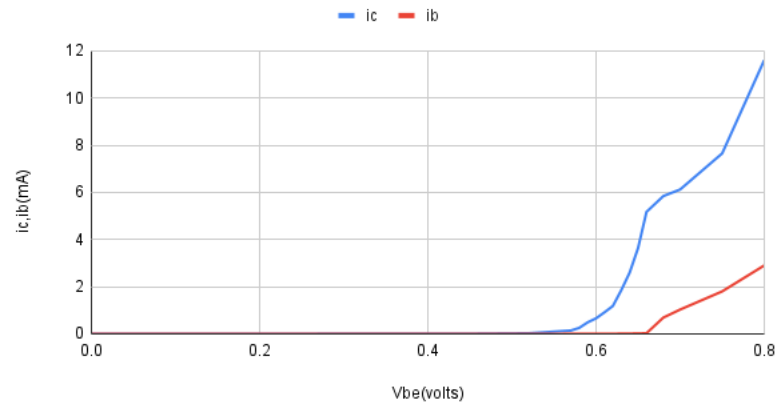


Figure 5: i_c, i_b vs V_{be}

ic,ib(log scale) vs Vbe (Gummel plot)

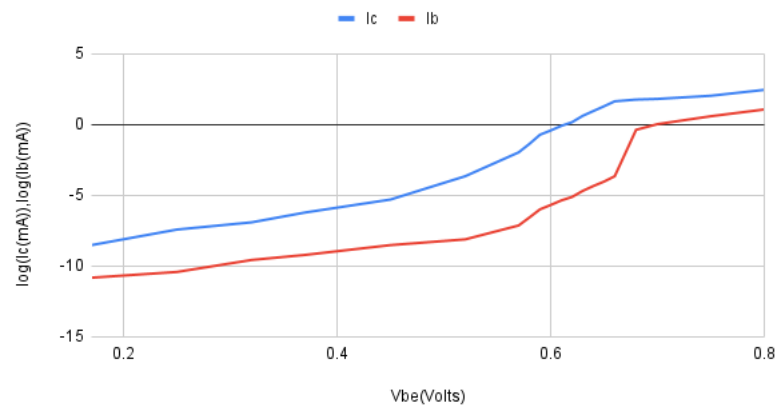


Figure 6: i_c, i_b (log scale) vs V_{be} (Gummel plot)

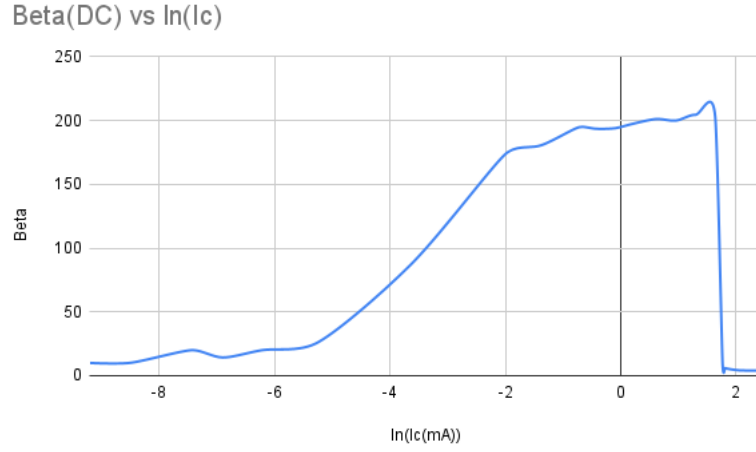


Figure 7: Beta(DC) vs ln(Ic)

4 Experimental results

BJT Parameters in CE configuration

As,

$$I_e = I_c + I_b \quad (1)$$

for each I_b we get different alpha and beta values.

$$\alpha = i_c / i_e \quad (2)$$

$$\beta = i_c / i_b \quad (3)$$

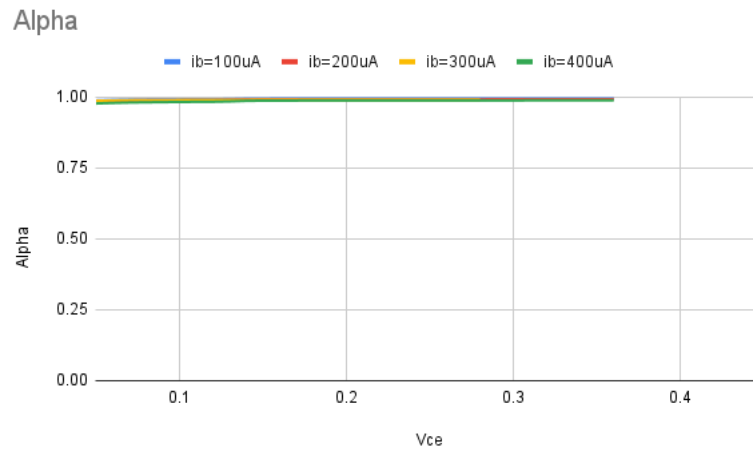


Figure 8: Alpha

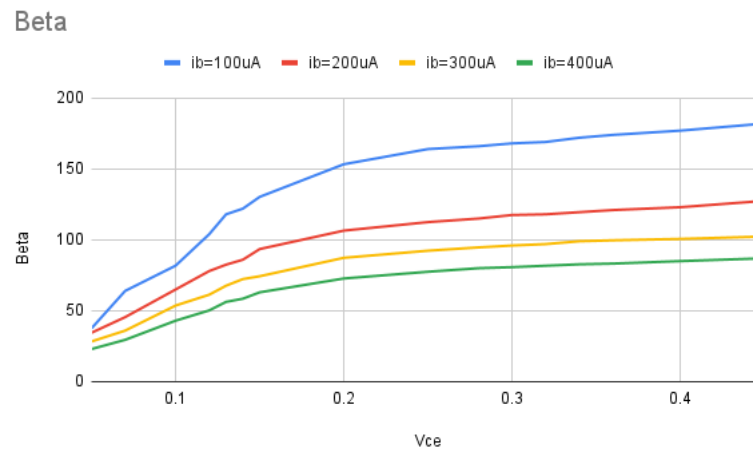


Figure 9: Beta

Alpha stayed approximately at .98 for different I_b values.
 Beta started quite low and increased as V_{ce} increases, and as we increase I_b beta value for a particular V_{ce} decreased.
 From extrapolating we got the early voltage as -1.253V

BJT Parameters in CB configuration

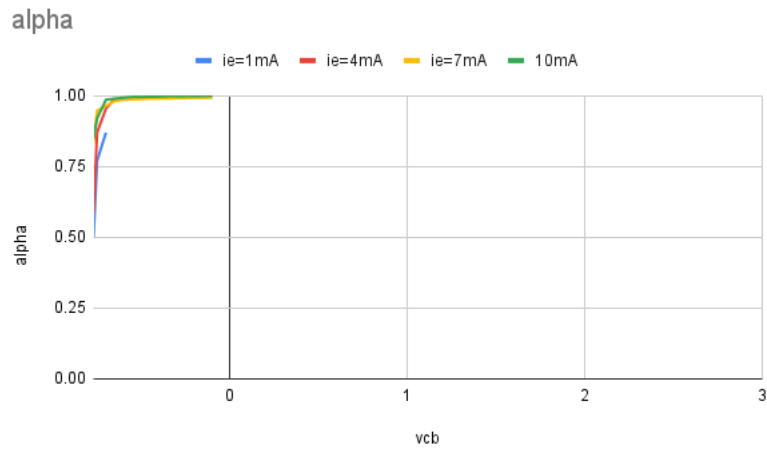


Figure 10: Alpha

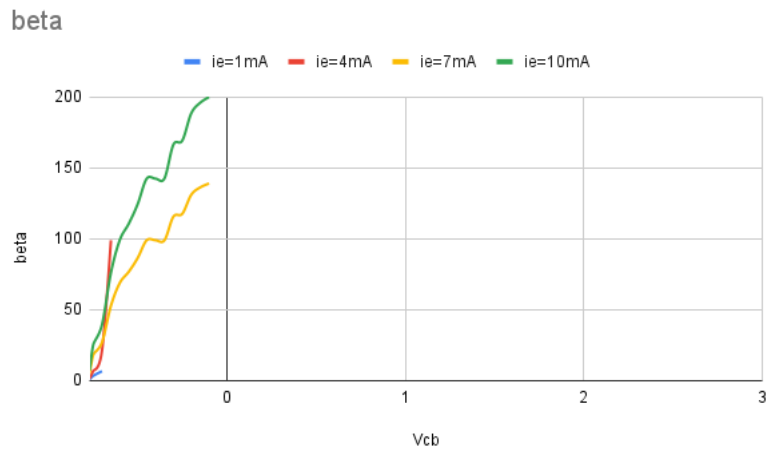


Figure 11: Beta

Here both alpha and beta are quite low at initial values of v_{cb} and increased later as v_{cb} increases.

Small Signal Parameters

$I_c = 4.5 \text{ mA}$ and $V_{ce}=5\text{V}$ we got:

$i_b=.02\text{mA}$

$g_m=I_c \cdot v_t = 4.5\text{mA} \cdot 0.026\text{V}=.117\text{m}$ Simon

$\beta=225$

$r_{pi}=26.325\text{e-}3$

5 Experiment completion status

The experiment was fully completed in the lab.